
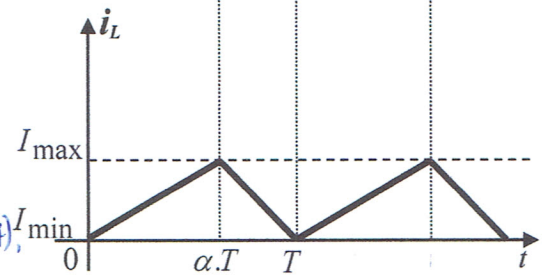
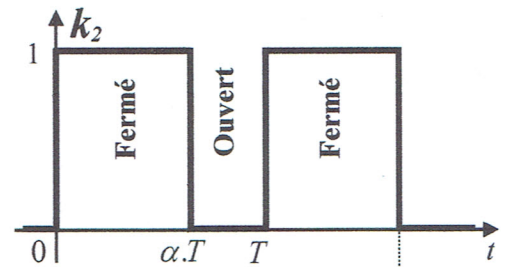


Corrigé type examen S05

28/01/2020

Durée : 1H30mn

Exercice N°01(08pts)

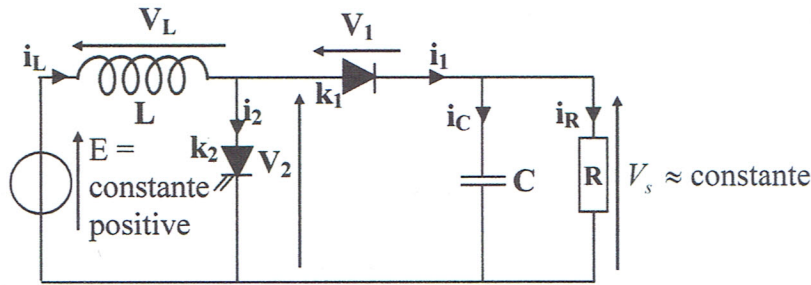

a) Dans ce montage, on a un régime à la limite de conduction.

b) Les allures des signaux de  $i_1(t)$ ,  $i_2(t)$  et  $V_2(t)$ .

c) - Pour  $t \in [0, \alpha T]$ ,  $i_1(t) = \frac{E}{L} t$  --- (1)

à  $t = \alpha T$ :  $i_1(\alpha T) = i_{max} = \frac{E}{L} \alpha T$  --- (2)

Pour  $t \in [\alpha T, T]$ :




$i_1(t) = \frac{E - V_s}{L} (t - \alpha T) + i_{max}$  --- (3)

à  $t = T$ :  $i_1(T) = \frac{E - V_s}{L} (T - \alpha T) + i_{max} = 0$  --- (4)

en substituant (2) dans (4), on aura:

$$\frac{E - V_s}{L} T(1 - \alpha) + \frac{E}{L} \alpha T = 0$$
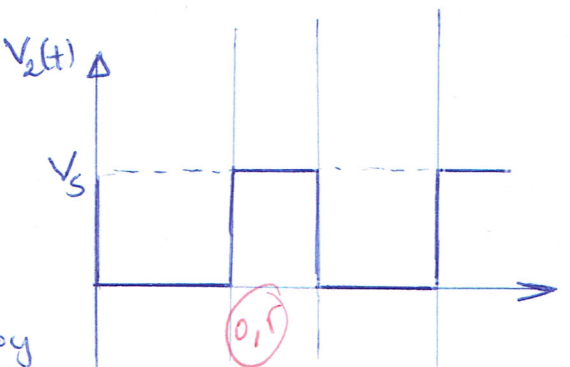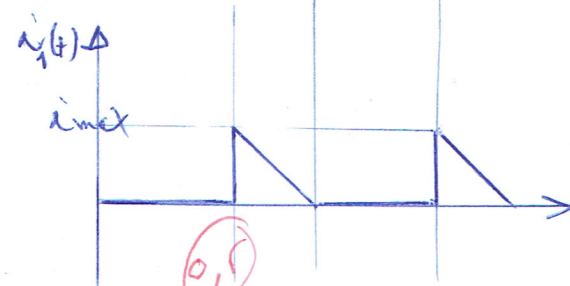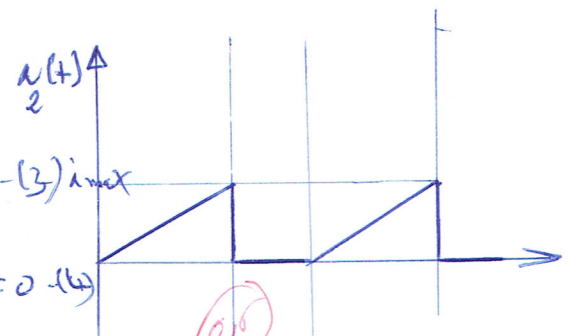
$$\Rightarrow V_s = \frac{E}{1 - \alpha}$$



d)  $i_{L\text{moy}} = \frac{i_{max}}{2}$

e)  $i_{1\text{moy}} = \frac{i_{L\text{moy}} (T - \alpha T)}{T}$

$$\Rightarrow i_{1\text{moy}} = i_{L\text{moy}} (1 - \alpha)$$

f) -  $i_{2\text{moy}} = \frac{i_{L\text{moy}} \cdot \alpha T}{T} = \alpha i_{L\text{moy}}$

$$\Rightarrow i_{2\text{moy}} = \alpha \cdot i_{L\text{moy}}$$

$$g) \cdot i_i(t) = i_c(t) + i_R(t) \Rightarrow i_{R\text{moy}} = i_{L\text{moy}} - i_{C\text{moy}}$$

$$\Rightarrow i_{R\text{moy}} = i_{L\text{moy}} = i_{L\text{max}}(1-\alpha) = \frac{i_{\text{max}}}{2}(1-\alpha)$$

$$\Rightarrow i_{R\text{moy}} = (1-\alpha) \cdot \frac{i_{\text{max}}}{2}$$

$$h) \cdot P_s = V_s \cdot i_R \Rightarrow P_{s\text{moy}} = \frac{E}{1-\alpha} \cdot \frac{i_{\text{max}}}{2} \cdot (1-\alpha) = E \cdot \frac{i_{\text{max}}}{2}$$

i) Par conservation de la puissance active :  $P_{\text{fournie}} = P_{\text{reçue}}$   
 $\Rightarrow (P_{\text{fournie}})_{\text{moy}} = (P_{\text{reçue}})_{\text{moy}}$



$$\Rightarrow P_{\text{fournie}} = P_{L\text{moy}} + P_{C\text{moy}} + P_{R\text{moy}} = P_{R\text{moy}}$$

$$\Rightarrow P_e = P_s = P_R$$


j)  $P_s = P_e \Rightarrow E \cdot i_{L\text{moy}} = V_s \cdot i_{L\text{moy}} = V_s \cdot i_{L\text{moy}}(1-\alpha)$

$$\Rightarrow V_s = \frac{E}{1-\alpha}$$

Exercice N ° 02 ( 7 pts)

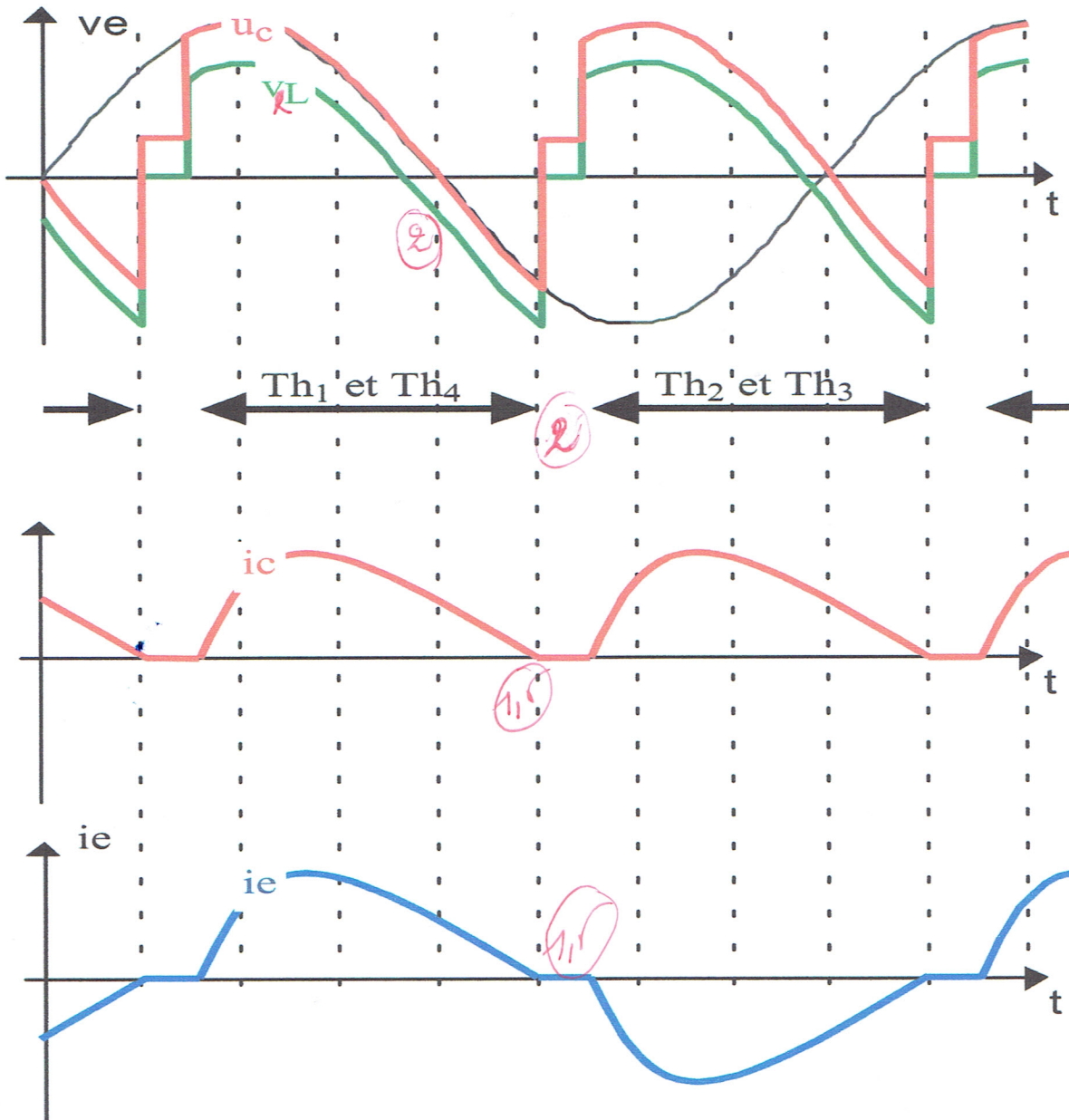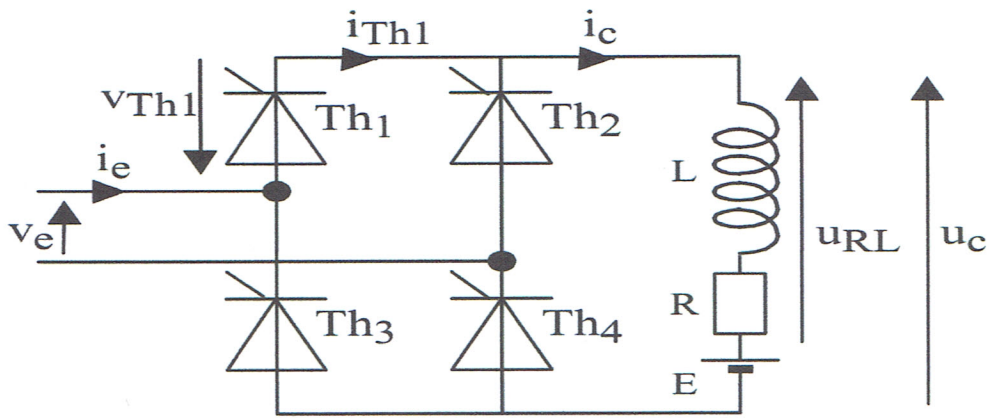


# **Exercice N°03 (05 pts)**

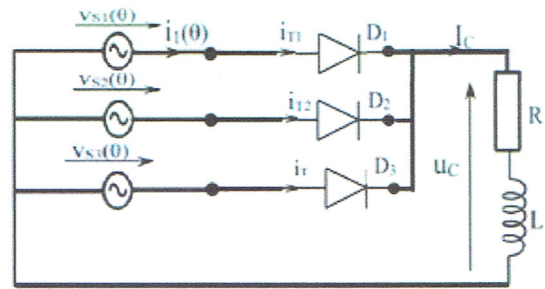

1- tableau d'analyse de fonctionnement du document réponse.

Intervalles	Diode en conduction	$U_{ch}$	$V_{D1}$	$i_{D1}$	$i_2$
$[0, \frac{\pi}{6}]$	D3	$V_3$	$U_{13}$	0	0
$[\frac{\pi}{6}, \frac{5\pi}{6}]$	D1	$V_1$	0	$I_c$	0
$[\frac{5\pi}{6}, \frac{3\pi}{2}]$	D2	$V_2$	$U_{12}$	0	$I_c$
$[\frac{3\pi}{2}, 2\pi]$	D3	$V_3$	$U_{13}$	0	0

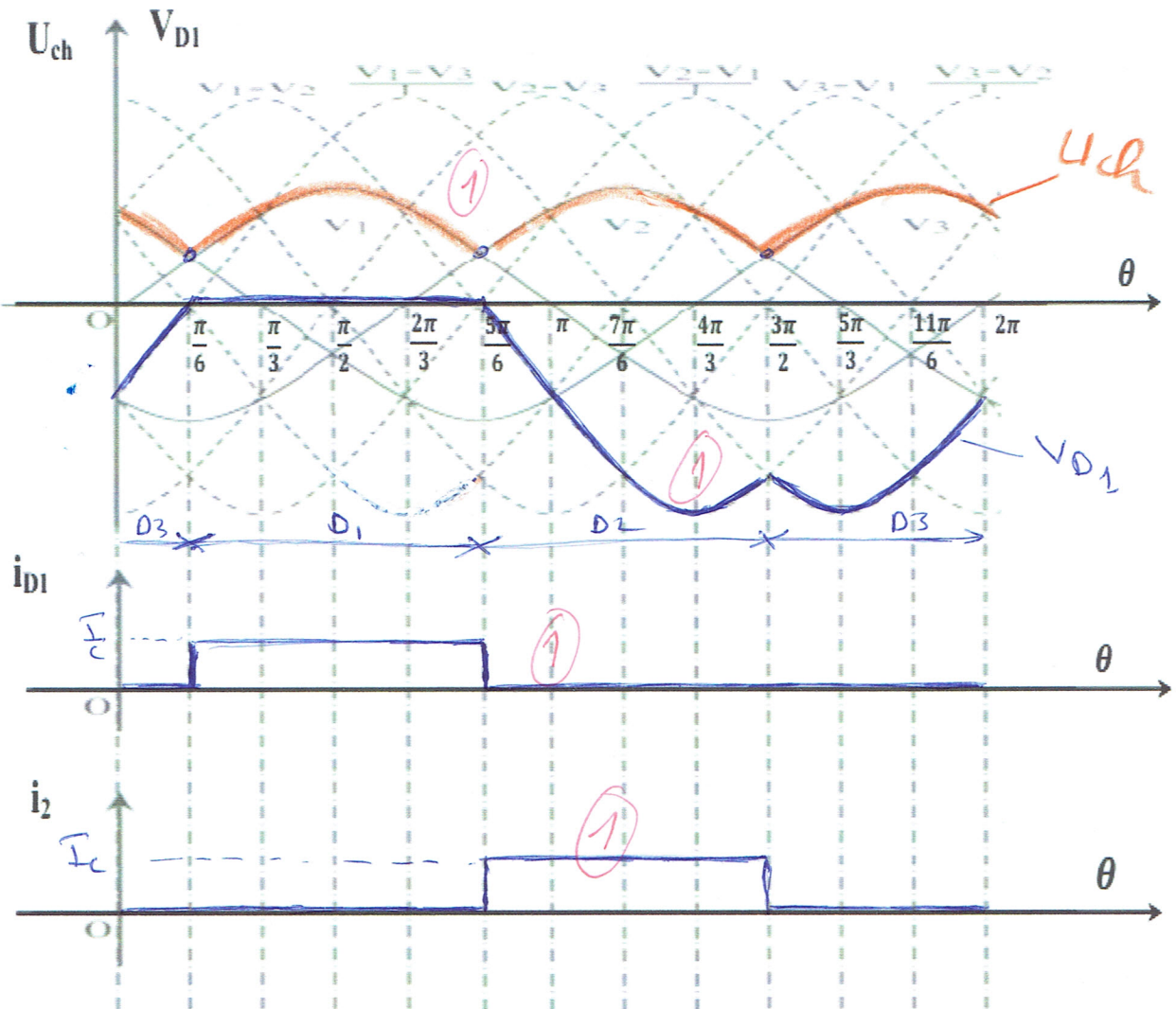2- Représentation des graphes :  $u_C(\theta)$ ,  $v_{D1}(\theta)$ ,  $i_{D1}(\theta)$  et  $i_2(\theta)$ .



$$3) - U_{\text{ch moy}} = \frac{3}{2\pi} \int_{\frac{\pi}{6}}^{\frac{5\pi}{6}} V_{\text{max}} \sin \theta d\theta.$$

$$= \frac{+3V_{\text{max}}}{2\pi} \left( -\cos \theta \right) \Big|_{\frac{\pi}{6}}^{\frac{5\pi}{6}}$$

$$= \frac{3V_{\text{max}}}{2\pi} \left( -\cos \frac{5\pi}{6} + \cos \frac{\pi}{6} \right)$$

$$= \frac{3V \cdot \sqrt{2}}{2\pi} \left( \frac{\sqrt{3}}{2} \right) = \frac{3V \cdot \sqrt{6}}{2\pi}$$

$$\Rightarrow U_{\text{ch moy}} = \frac{3V \cdot \sqrt{6}}{2\pi}$$

$$\bullet \text{ Si } U_{\text{ch moy}} = 256 \text{ V} \Rightarrow \frac{3V \cdot \sqrt{6}}{2\pi} = 256$$

$$\Rightarrow V = \frac{2\pi \times 256}{3 \cdot \sqrt{6}}$$

$$\Rightarrow V = 218,88 \text{ V}$$