

## EXAMEN D'ELECTROTECHNIQUE FONDAMENTALE I

### EXERCICE 1 (7 pt)

Soit le circuit suivant Fig. 1 :

- Calculer les courants  $I_1$ ,  $I_2$  et  $I_3$ .
- Tracer le diagramme des phaseurs  $E$ ,  $I_1$ ,  $I_2$ ,  $I_3$  et trois tensions des branches ( $V_{Z1}$ ,  $V_{Z2}$  et  $V_{Z3}$ ).
- Calculer les puissances active, réactive et apparente dans les trois branches.
- Quelles sont les puissances réelle, réactive et apparente fournies par la source ?
- Quel est le facteur de puissance vu par la source ?

### EXERCICE 2 (7 pt) Fig. 2

On a monté en triangle, trois charges identiques résistance de  $25 \Omega$ , inductance de  $0.15 H$  et capacité de  $120 \mu F$  en série sur un réseau triphasé de tension entre lignes de  $400V - 50 Hz$ .

- Déterminer les courants de ligne et de phase et la puissance active, réactive et apparente totale.

### EXERCICE 3 (6 pt)

Entre les trois bornes 1, 2, 3 on dispose d'un système de tensions composées  $U_{12}$ ,  $U_{23}$ ,  $U_{31}$  formant un système triphasé déséquilibré.

Les tensions homopolaire  $V_0$ , directe  $V_d$  et inverse  $V_i$  sont liées aux tensions simples par les relations :

$$\begin{cases} V_0 = \frac{1}{3}(V_a + V_b + V_c) \\ V_d = \frac{1}{3}(V_a + a V_b + a^2 V_c) \\ V_i = \frac{1}{3}(V_a + a^2 V_b + a V_c) \end{cases}, \text{ avec } a = e^{j\frac{2\pi}{3}} = 1 \angle 120^\circ$$

$$\begin{bmatrix} V_0 \\ V_d \\ V_i \end{bmatrix} = \frac{1}{3} \begin{bmatrix} 1 & 1 & 1 \\ 1 & a & a^2 \\ 1 & a^2 & a \end{bmatrix} \begin{bmatrix} V_a \\ V_b \\ V_c \end{bmatrix}$$

- Calculer la quantité :  $1 + a + a^2$
- En déduire que  

$$U_{12} - a^2 U_{23} = 3V_d$$

$$U_{12} - a U_{23} = 3V_i$$
- Déterminer par construction graphique des composantes  $V_0$ ,  $V_d$  et  $V_i$  si  
 $V_a = 200 \angle 0^\circ$ ;  $V_b = 200 \angle -90^\circ$   $V_c = 200 \angle 135^\circ$

### EXERCICE 4 (6 pt) Fig 3

Un circuit  $RC$  série  $R = 5 \Omega$  et  $C = 80 mF$ , est alimenté par une tension constante  $V = 10 V$  à l'instant  $t = 0 s$  où l'interrupteur est fermé.

- Ecrire l'équation différentielle donnant  $i$ ,  $v_R$  et  $v_C$
- Calculer le courant à l'instant  $t = 1 s$
- Calculer le temps au bout duquel  $v_R = v_C$

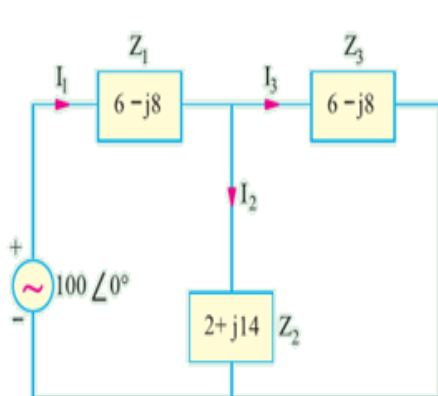


Fig1

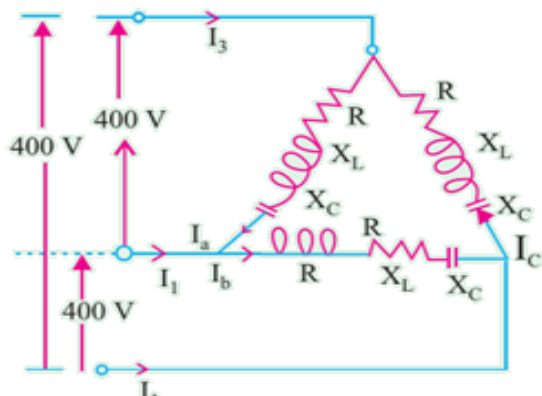


Fig 2

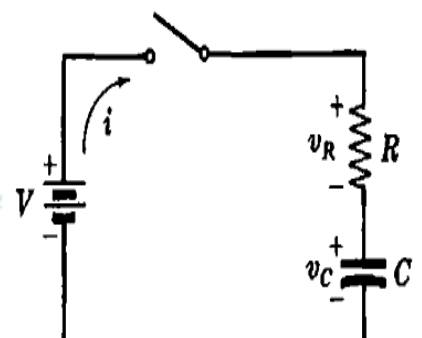


Fig 3

**Solution.**  $Z_1 = 6 - j8 = 10 \angle -53.13^\circ$ ;  $Z_2 = 2 + j14 = 14.14 \angle 81.87^\circ$ ;  $Z_3 = 6 - j8 = 10 \angle -53.13^\circ$

$$Z_{23} = \frac{Z_2 Z_3}{Z_2 + Z_3} = 14.14 \angle -8.13^\circ = 14 - j2$$

Drop across two parallel impedances is given by

$$V_{23} = 100 \frac{14 - j2}{(6 - j8) + (14 - j2)} = 63.2 \angle 18.43^\circ = 60 + j20$$

$$V_1 = 100 \frac{10 \angle -53.13^\circ}{6 - j8 + (14 - j2)} = 44.7 \angle -26.57^\circ = 40 - j20$$

$$I_1 = \frac{44.7 \angle -26.57^\circ}{10 \angle -53.13^\circ} = 4.47 \angle 26.56^\circ$$

$$I_2 = \frac{63.2 \angle 18.43^\circ}{14.14 \angle 81.87^\circ} = 4.47 \angle -63.44^\circ$$

$$I_3 = \frac{63.2 \angle 18.43^\circ}{10 \angle -53.13^\circ} = 6.32 \angle 71.56^\circ$$


$$P_1 = V_1 I_1 \cos \phi_1 = 44.7 \times 4.47 \times \cos 53.13^\circ = 120 \text{ W}$$

$$P_2 = V_2 I_2 \cos \phi_2 = 63.2 \times 4.47 \times \cos 81.87^\circ = 40 \text{ W};$$

$$P_3 = V_3 I_3 \cos \phi_3 = 63.2 \times 6.32 \times \cos 53.13^\circ = \mathbf{240 \text{ W}}, \text{ Total} = 400 \text{ W}$$

As a check, power delivered by the 100-V source is,

$$P = V I_1 \cos \phi = 100 \times 4.47 \times \cos 26.56^\circ = 400 \text{ W}$$

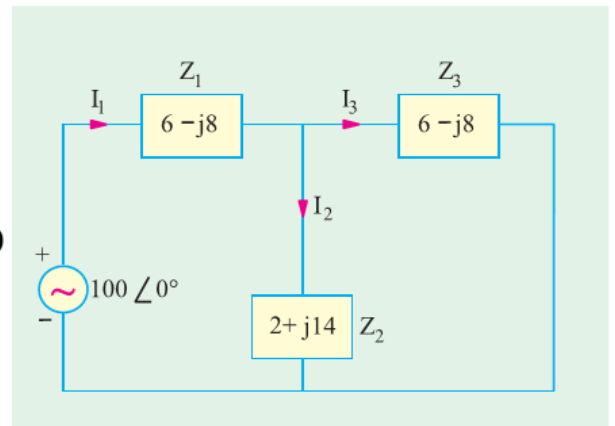

**Fig. 14.41**

**Example 14.44.** For the circuit in Fig. 14.47 (a), given that  $L = 0.159 \text{ H}$

$$C = 0.3183 \text{ mf}$$


$$I_2 = 5 \angle 60^\circ \text{ A}$$

$$V_1 = 250 \angle 90^\circ \text{ volts.}$$

**Find :-**

- (i) Impedance  $Z_1$  with its components.
- (ii) Source voltage in the form of  $V_m \cos (\omega t + \phi)$ .
- (iii) Impedance  $Z_2$  with its components so that source p.f. is unity, without adding to the circuit power loss.
- (iv) Power loss in the circuit
- (v) Draw the phasor diagram.

**(Bombay University 1997)**

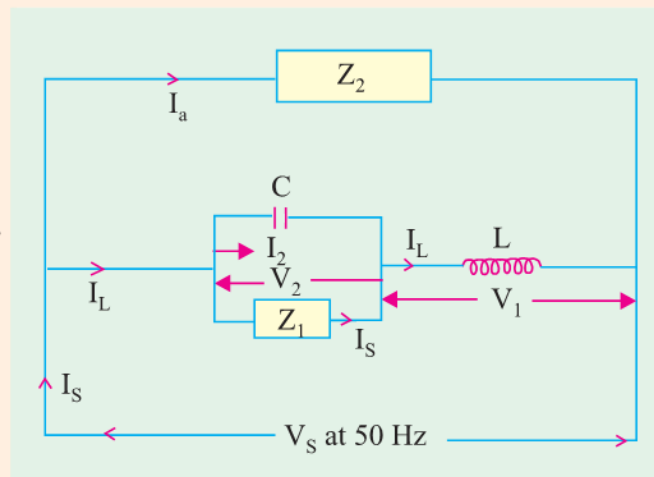

**Fig. 14.47 (a)**

**Solution.**  $X_L = 314 \times 0.159 = 50 \text{ ohms}$

$$X_C = 1/(314 \times 0.3183 \times 10^{-3}) = 10 \text{ ohms}$$

$$I_L = V_1/X_L = (250 \angle 90^\circ) / (50 \angle 90^\circ) = 5 \angle 0^\circ \text{ amps}$$

$$V_2 = -jI_2 X_C = (5 \angle 60^\circ) \times (10 \angle -90^\circ) = 50 \angle -30^\circ \text{ volts} = 43.3 - j25 \text{ volts}$$

$$\begin{aligned} I_L &= I_L - I_2 = 5 \angle 0^\circ - 5 \angle 60^\circ = 5 + j0 - 5(0.5 + j0.866) \\ &= 2.5 - j4.33 = 5 \angle -60^\circ \end{aligned}$$

(a)  $Z_1 = V_2/I_1 = (50 \angle -30^\circ) / 5 \angle -60^\circ = 10 \angle +30^\circ$   
 $= 10 (\cos 30^\circ + j \sin 30^\circ) = 8.66 + j5$

(b)  $V_s = V_1 + V_2 = 0 + j250 + 43.3 - j25 = 43.3 + j225$   
 $= 229.1 \angle 79.1^\circ \text{ volts}$

$$V_s \text{ has a peak value of } (229.1 \times \sqrt{2}) = 324 \text{ volts}$$

$$V_s = 324 \cos (314 t - 10.9^\circ), \text{ taking } V_1 \text{ as reference}$$

or  $V_s = 325 \cos (314 t - 79.1^\circ), \text{ taking } I_L \text{ as reference.}$

(c) Source Current must be at unity P.f., with  $V_s$

$$\text{Component of } I_L \text{ in phase with } V_s = 5 \cos 79.1^\circ = 0.9455 \text{ amp}$$

$$\begin{aligned} \text{Component of } I_L \text{ in quadrature with } V_s \text{ (and is lagging by } 90^\circ) \\ = 5.00 \times \sin 79.1^\circ = 4.91 \text{ amp} \end{aligned}$$

$Z_2$  must carry  $I_a$  such that no power loss is there and  $I_s$  is at unity P.f. with  $V_s$ .

$I_a$  has to be capacitive, to compensate, in magnitude, the quadrature component of  $I_L$

$$|I_a| = 4.91 \text{ amp}$$

$$|Z_2| = V_s / |I_a| = 229.1/4.91 = 46.66 \text{ ohms}$$

$$\text{Corresponding capacitance, } C_2 = 1 / (46.66 \times 314) = 68.34 \mu\text{F}$$

(d) Power-loss in the circuit  $= I_1^2 \times 8.66 = 216.5 \text{ watts}$  or power  $= V_s \times \text{component of } I_L \text{ in phase with } V_s = 299.1 \times 0.9455 = 216.5 \text{ watts}$

(e) Phasor diagram is drawn in Fig. 14.47 (b)

**Example 23.2.** Explain how an unsymmetrical system of 3-phase currents can be resolved into 3 symmetrical component systems.

Determine the values of the symmetrical components of a system of currents

$$I_R = 0 + j120A; I_Y = 50 - j100A; I_B = -100 - j50A$$

Phase sequence is RYB.

(Elect. Engg.-I Bombay, Univ.)

**Solution.**  $\mathbf{I}_R \quad 0 \quad j120 \quad 120 \quad 90$

$$\mathbf{I}_Y \quad 50 \quad j100 \quad 111.8 \quad 63.5 ; \mathbf{I}_B \quad 100 \quad j50 \quad 111.8 \quad 153.5$$

(i) Positive-sequence Components

$$\mathbf{I}_1 = \frac{1}{3}(\mathbf{I}_R + a\mathbf{I}_Y + a^2\mathbf{I}_B) = \frac{1}{3}(0 + j120) + \frac{1}{2}j\frac{\sqrt{3}}{2}(50 - j100) + \frac{1}{2}j\frac{\sqrt{3}}{2}(-100 - j50)$$

$$= 22.8 + j108.3 = 110.7 \angle 78.1^\circ \therefore \mathbf{I}_{R1} \quad 110.7 \quad 78.1 ; \mathbf{I}_{Y1} \quad 110.7 \quad 41.9 ; \mathbf{I}_{B1} \quad 110.7 \quad 198.1$$

**(ii) Negative-sequence components**

$$\mathbf{I}_2 = \frac{1}{3}(\mathbf{I}_R + a^2 \mathbf{I}_Y + a \mathbf{I}_B) = \frac{1}{3}(18.3 - j65.1 + 6.1 - j21.7 - 22.5 - j105.7)$$


$$\therefore \mathbf{I}_{R2} = 22.5 - j105.7 ; \mathbf{I}_{Y2} = 22.5 - j22.5 ; \mathbf{I}_{B2} = 22.5 - j14.3$$

**(iii) Zero-sequence component**

$$\mathbf{I}_0 = \frac{1}{3}(\mathbf{I}_R + \mathbf{I}_Y + \mathbf{I}_B) = \frac{1}{3}[(0 - j120) + (50 - j100) + (100 - j50)] = 16.7 - j10$$

As a check, it may be found that

$$\mathbf{I}_R = \mathbf{I}_{R1} + \mathbf{I}_{R2} + \mathbf{I}_0; \mathbf{I}_Y = \mathbf{I}_{Y1} + \mathbf{I}_{Y2} + \mathbf{I}_0; \mathbf{I}_B = \mathbf{I}_{B1} + \mathbf{I}_{B2} + \mathbf{I}_0$$

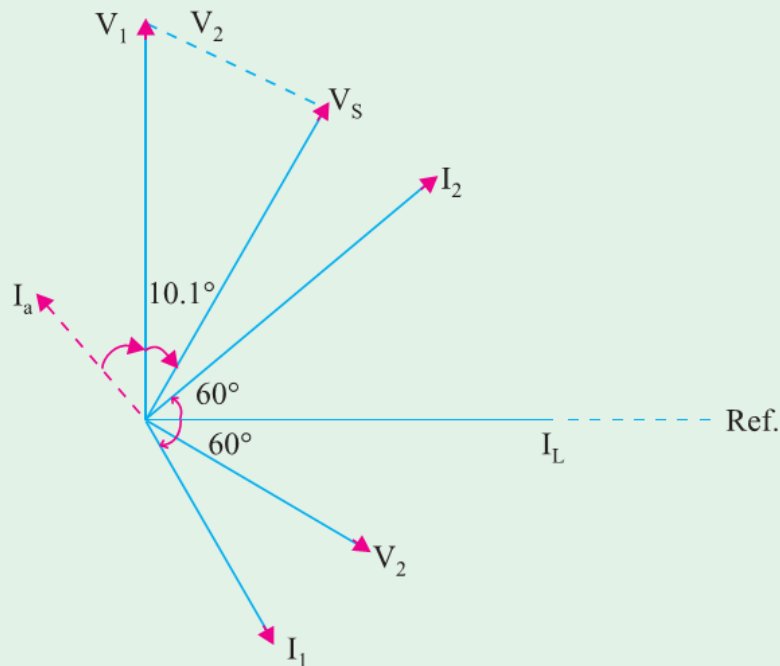

**Fig. 14.47 (b)** Phasor diagram

**Example 19.10.** A three phase 400-V, 50 Hz, a.c. supply is feeding a three phase delta-connected load with each phase having a resistance of 25 ohms, an inductance of 0.15 H, and a capacitor of 120 microfarads in series. Determine the line current, volt-amp, active power and reactive volt-amp. **[Nagpur University, November 1999]**

## EXERCICE 2

On a monté en triangle, trois charges identiques résistance de 25 Ω, inductance de 0.15 H et capacité de 120 μF en série sur un réseau triphasé de tension entre lignes de 400V - 50 Hz

Déterminer le courant de ligne et de phase et les puissance actives, réactive et apparente

**Solution.** Impedance per phase  $r + jX_L - jX_C$

$$X_L = 2\pi \times 50 \times 0.15 = 47.1 \, \Omega$$

$$X_C = \frac{10^6}{32.37} = 26.54 \, \Omega$$

$\cos \phi = \frac{25}{32.37}$  Lagging, since inductive reactance is dominating.

$$\text{Phase Current} = \frac{400}{25 + j20.56} = 12.357$$

$$\text{Line Current} = \sqrt{3} \times 12.357 = 21.4 \text{ amp}$$


Since the power factor is 0.772 lagging,

$$P = \text{total three phase power} = \sqrt{3} V_L I_L \cos \phi \times 10^{-3} \text{ kW}$$

$$= \sqrt{3} \times 400 \times 21.4 \times 0.772 \times 10^{-3} = 11.446 \text{ kW}$$

$$S = \text{total 3 ph kVA} \frac{11.446}{0.772} = 14.83 \text{ kVA } 14.83 \text{ kVA}$$

$$Q = \text{total 3 ph "reactive kilo-volt-amp"} \sqrt{3} = (S^2 - P^2)^{0.50} = 9.43 \text{ kVAR lagging}$$

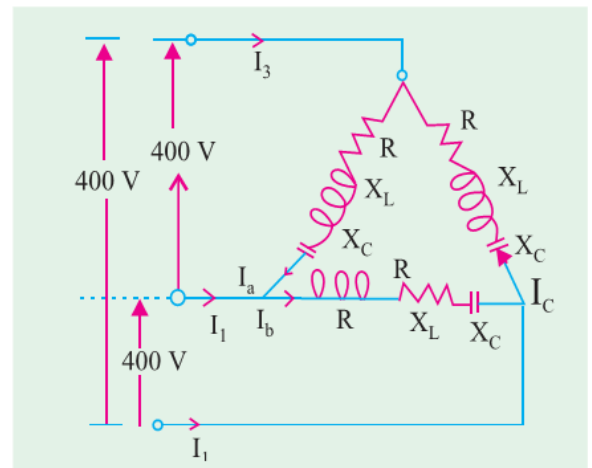

**Fig. 19.22**